

BEST AVAILABLE COPY

# THE DESIGN OF CMOS RADIO-FREQUENCY INTEGRATED CIRCUITS

SECOND EDITION

THOMAS H. LEE

*Stanford University*



CAMBRIDGE  
UNIVERSITY PRESS

EXHIBIT A

PUBLISHED BY THE PRESS SYNDICATE OF THE UNIVERSITY OF CAMBRIDGE  
The Pitt Building, Trumpington Street, Cambridge, United Kingdom

CAMBRIDGE UNIVERSITY PRESS  
The Edinburgh Building, Cambridge CB2 2RU, UK  
40 West 20th Street, New York, NY 10011-4211, USA  
477 Williamstown Road, Port Melbourne, VIC 3207, Australia  
Ruiz de Alarcón 13, 28014 Madrid, Spain  
Dock House, The Waterfront, Cape Town 8001, South Africa  
<http://www.cambridge.org>

© Cambridge University Press 1998  
© Thomas H. Lee 2004

This book is in copyright. Subject to statutory exception and  
to the provisions of relevant collective licensing agreements,  
no reproduction of any part may take place without  
the written permission of Cambridge University Press.

First published 1998  
Second edition first published 2004

Printed in the United States of America

*Typeface* Times 10.75/13.5 and Futura *System* AMS-TEX [FH]

*A catalog record for this book is available from the British Library.*

*Library of Congress Cataloging in Publication data*  
Lee, Thomas H., 1959–

The design of CMOS radio-frequency integrated circuits / Thomas H. Lee. – 2nd ed.  
p. cm.

ISBN 0-521-83539-9

1. Metal oxide semiconductors, Complementary – Design and construction. 2. Radio  
frequency integrated circuits – Design and construction. 3. Radio – Transmitter-receivers.  
I. Title.

TK7871.99.M44L44 2004  
621.39'732 – dc22

2003061322

ISBN 0 521 83539 9 hardback

drain currents, and hence that of the NMOS  $V_{gs}$ . Thus, the diode voltage appears across  $R$ ; the corresponding current is the same in both halves of the mirror and is therefore the bias current of the diode itself. Thus, as in the op-amp version of this circuit, the diode provides its own bias current.

The self-biased circuit of Figure 10.4 is quite versatile. It should be clear that the diode may be replaced by a variety of elements. For example, a diode-connected MOSFET would produce a bias current of  $V_{gs}/R$ , or a zener diode (if available) could be used instead. As we'll see in the next section, the self-biased circuit is particularly useful in realizing bandgap voltage references in CMOS technology. Some minor subtleties concerning the operation of the quad of MOSFETs in Figure 10.4 are considered in Problem 12.

### 10.5 BANDGAP VOLTAGE REFERENCE

Because IC technology directly offers no reference voltages that are inherently constant, the only practical option is to combine two voltages with precisely complementary temperature behavior. Thus, the general recipe for making temperature-independent references is to add a voltage that goes up with temperature to one that goes down with temperature. If the two slopes cancel, the sum will be independent of temperature.

Without question, the most elegant realization of this idea is the bandgap voltage reference. It produces an output voltage that is traceable to fundamental constants and therefore relatively insensitive to variations in process, temperature, and supply.

The first widely used bandgap voltage reference was designed by Bob Widlar in the hugely popular and revolutionary LM309 5-V regulator IC from National Semiconductor. It was the first reference whose initial accuracy was good enough to eliminate the requirement for adjustment by the end user. Thus, only three terminals were needed (allowing use of inexpensive transistor packages), making this part as easy to use as one could hope.

To understand quantitatively how bandgap references work, we need to re-examine the detailed behavior of junction voltage with temperature. Since transistor junctions exhibit more nearly ideal characteristics than ordinary diodes, we will assume bandgap implementations that use transistors. A plot of  $V_{BE}$  versus temperature is sketched in Figure 10.5.<sup>6</sup>

Recall that  $V_{BE}$  is nearly perfectly CTAT (i.e., it goes down linearly with temperature). Now suppose we add to this CTAT  $V_{BE}$  a voltage that is perfectly proportional to absolute temperature (PTAT). If we choose the slope of the PTAT term equal in magnitude to that of the CTAT term, the sum will be independent of temperature (see Figure 10.6). We see that something funny happens above about 600 K, but the fact

<sup>6</sup> Again, keep in mind that this plot of  $V_{BE}$  is a slight fiction because we have neglected the small curvature caused by the weak temperature dependence of  $I_0$ . The correction is second-order, and we will take care of this little detail shortly.

$V_{GO}$

$V_{GC}$

that the pr.  
concern.

Note th  
output eqt  
ature. Sta  
voltage eq  
temperatu

At this  
whole cor  
for  $V_{BE}$ :

Using this  
transistor:

 
 
FIGURE 10.5.  $V_{BE}$  versus temperature.

FIGURE 10.6. Illustration of bandgap reference principle.

that the principle fails at temperatures high enough to melt lead is rarely a practical concern.

Note that the addition of a PTAT and CTAT voltage in the proper ratio yields an output equal to the bandgap voltage (extrapolated to 0 K), independent of temperature. Stated another way, if we adjust the PTAT component to make the output voltage equal to  $V_{GO}$  at any temperature, then the output voltage will equal  $V_{GO}$  at all temperatures – at least in this slightly simplified picture.

At this point, it's natural to consider how one obtains a PTAT voltage, since this whole concept relies on having one around. Let's start with the familiar equation for  $V_{BE}$ :

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right). \quad (5)$$

Using this expression, we can readily compute the *difference* in two  $V_{BE}$ s for identical transistors operating at two different values of collector current (or, more generally,

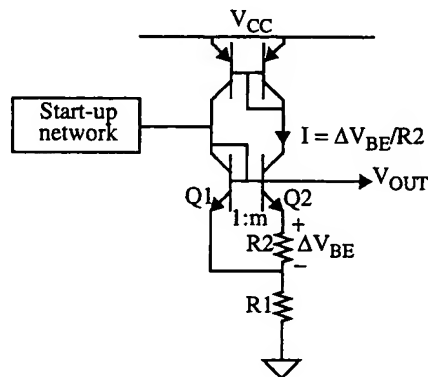


FIGURE 10.7. Classic Brokaw bandgap reference circuit.

for transistors made in the same process, operating at two different values of collector current density):

$$\Delta V_{BE} = V_{BE2} - V_{BE1} = V_T \ln \left( \frac{J_{C2}}{J_{C1}} \right). \quad (6)$$

The misleading  $I_S$  term drops out, so we can conclude confidently that  $\Delta V_{BE}$  truly is PTAT if the collector current densities are in a fixed ratio. Thus, while each  $V_{BE}$  is nearly CTAT, the *difference* between two  $V_{BE}$ s is perfectly PTAT.

### 10.5.1 CLASSIC BANDGAP REFERENCE

Now that we've got all the ingredients, all that remains is to sum the CTAT  $V_{BE}$  term with the right amount of PTAT  $\Delta V_{BE}$ . Although one could imagine a number of methods for doing so, the Brokaw cell is a particularly elegant (and accurate) implementation of the bandgap reference. The classic bipolar implementation is shown in Figure 10.7 (again, basic mirrors are shown for simplicity's sake); we'll modify this circuit shortly for implementation in CMOS technology.

As we shall see, the output voltage is the sum of a PTAT voltage and a  $V_{BE}$ . Here,  $Q_1$  and  $Q_2$  operate at a fixed current density ratio of  $m$  ( $>1$ ) set, for example, by ratioing the emitter areas. Now, by KVL, the voltage across  $R_2$  is the difference in  $V_{BE}$ s of  $Q_1$  and  $Q_2$ , and is therefore PTAT and equal to  $V_T \ln m$ . Assuming that the TC of  $R_2$  is negligibly small, the current passing through it will also be PTAT. Furthermore, the current through  $R_1$  is simply twice that through  $R_2$ , since the two collector currents are equal.<sup>7</sup> Therefore, the voltage drop across the entire resistor string is purely PTAT. Finally, the output voltage is just this PTAT voltage plus the  $V_{BE}$  of  $Q_2$ , as advertised. With proper choice of  $R_1$  and  $R_2$ , the output voltage will have zero TC. As a free bonus, a PTAT voltage is available at the emitters of  $Q_1$  and  $Q_2$ , providing thermometer outputs.

<sup>7</sup> We are neglecting errors due to mismatch, nonzero base currents, and finite Early voltage.

To carry out :  
As a specific c  
and  $100 \mu\text{A}$  f  
sets  $\Delta V_{BE} =$   
at 300 K. Sin  
the collector  
value of  $R_2 =$   
 $1.2 \text{ V}$ , the dro  
the current th  
 $R_1 = 0.496 \text{ V}$

You may h  
stant (in fact  
why this doe  
time to take  
endency of  $I_0$ .

A quasien

where  $A_E$  is  
temperature,  
cient. For th  
has a value  
doped<sup>9</sup>) diff  
processes, r

With this

Plotting in F  
r the curvati

Because  
coefficient c  
havior for V  
reference in  
actual TC tl  
consider a c

<sup>8</sup> It is importa  
allel device  
due to proc

<sup>9</sup> Bandgap ne  
high values

### Design Example

To carry out an actual design, we need some characterization data for our process. As a specific example, suppose we go to the lab and find that  $V_{BE} = 0.65$  V at 300 K and  $100 \mu\text{A}$  for a transistor of  $Q_2$ 's size. Furthermore, let  $m = 8$ . This choice<sup>8</sup> of  $m$  sets  $\Delta V_{BE} = 53.8$  mV (a number comfortably larger than any offsets that we expect) at 300 K. Since we definitely know the value of  $V_{BE}$  at  $100 \mu\text{A}$ , a prudent choice for the collector currents would be this value of  $100 \mu\text{A}$ , and this choice then fixes the value of  $R_2 = \Delta V_{BE}/100 \mu\text{A} = 538 \Omega$ . Now, since we want the output voltage to be 1.2 V, the drop across  $R_1$  must be  $1.2 - V_{BE} - \Delta V_{BE} = 0.496$  V. Finally, noting that the current through  $R_1$  is twice that through  $R_2$ , we conclude that we should choose  $R_1 = 0.496 \text{ V}/200 \mu\text{A} = 2.48 \text{ k}\Omega$ , completing the design.

You may have noticed that the collector currents in the Brokaw cell are not constant (in fact, they are PTAT if we assume that the resistors have zero TC). To see why this does not invalidate all we've done so far (in fact, it is beneficial), it is now time to take care of a few details – namely, those involving the temperature dependency of  $I_0$ .

A quasiempirical expression for  $I_0$  is

$$I_0 = A_E B T^r, \quad (7)$$

where  $A_E$  is the emitter area,  $B$  is a process-dependent constant,  $T$  is the absolute temperature, and  $r$  is a process-dependent quantity we'll call the *curvature coefficient*. For the relatively deep, diffused emitters of older bipolar processes,  $r$  typically has a value between 2 and 3, while for the shallow, implanted (and very heavily doped<sup>9</sup>) diffusions that are more common in modern CMOS and high-speed bipolar processes,  $r$  typically ranges from 4 to 6.

With this equation for  $I_0$ , we can express  $V_{BE}$  as follows:


$$V_{BE} = V_{G0} - V_T \ln \left( \frac{A_E B T^r}{I_C} \right). \quad (8)$$

Plotting in Figure 10.8 as before, we can see why it is reasonable to call the parameter  $r$  the curvature coefficient (aside from the euphonious alliteration).

Because the argument of the log is not quite independent of  $T$ , the temperature coefficient of  $V_{BE}$  is not quite constant, leading to a small departure from CTAT behavior for  $V_{BE}$ . Additionally, we've seen at least one implementation of a bandgap reference in which the collector current is also not constant. So, let's compute the actual TC that results if, in addition to the temperature dependence of  $I_0$ , we also consider a collector current that varies as the  $n$ th power of  $T$ :

<sup>8</sup> It is important that  $Q_2$  be laid out as eight instances of  $Q_1$  to guarantee that  $Q_2$  behaves as eight parallel devices of  $Q_1$ 's size. If  $Q_1$  is placed at the center of a common-centroid arrangement, errors due to process variation will be minimized.

<sup>9</sup> Bandgap narrowing and nonlinearity in the heavily doped emitters are probably responsible for the high values of  $r$ .

 FIGURE 10.8.  $V_{BE}$  versus temperature.

$$\frac{dV_{BE}}{dT} = \frac{d}{dT} \left[ V_T \ln \left( \frac{CT^n}{A_E BT^r} \right) \right] = \frac{d}{dT} \left[ V_T \ln \left( \frac{C}{A_E BT^{r-n}} \right) \right], \quad (9)$$

so that

$$\frac{dV_{BE}}{dT} = \frac{k}{q} \left[ \ln \left( \frac{C}{A_E BT^{r-n}} \right) - (r-n) \right], \quad (10)$$

which we may rewrite in a somewhat lower-entropy form, as in Section 10.2:

$$\frac{dV_{BE}}{dT} = - \frac{[V_{G0} - V_{BE} + (r-n)V_T]}{T}. \quad (11)$$

Note that the curvature term disappears if  $r = n$ , and we're left with the same expression for the temperature coefficient as derived earlier. In the Brokaw cell,  $n = 1$ , which reduces the effect of yet does not cancel  $r$  (remember,  $r$  is typically a minimum of 2, and can range up to about 6). Graphically, think of the increasing collector current with temperature as straightening out the  $V_{BE}$  curve.

The next question is: How does the curvature term affect the bandgap reference itself? The most expedient answer comes from deriving the condition for net zero TC. Suppose we call  $GV_T$  the PTAT component that we add to  $V_{BE}$ . Then the TC of the PTAT component may be written as  $GV_T/T$ , so the condition for zero TC is

$$\frac{dV_{BE}}{dT} + \frac{GV_T}{T} = 0 \implies G = \frac{[V_{G0} - V_{BE} + (r-n)V_T]}{V_T}, \quad (12)$$

which corresponds to an output voltage of

$$V_{out}|_{TC=0} = V_{BE} + GV_T = V_{G0} + (r-n)V_T. \quad (13)$$

This last equation depends on  $V_T$  and therefore implies that the output voltage cannot have zero TC at all temperatures; the best we can do is achieve zero TC at one temperature. Furthermore, in order to achieve this zero-TC condition at that one temperature, we need to adjust the output to a voltage *higher* than  $V_{G0}$  by an amount equal to  $(r-n)V_T$ . Fortunately, this correction term is relatively small, typically amounting

to just tens of mV, so we need only be concerned where zero TC occurs.

At this point, it's fortunate, although they aren't quite perfect, that the output reference temperature value at this reference  $V_{out}$  as follows:

or, as some prefer,

Note that this output voltage is able to arrange the voltage would be at any temperature; curvature-correction.

Even without curvature inherent in the tributes little else one could expect +50°C and if it

As is evident, the temperature output is a matter of this temperature.

Table 10.1. Output voltage as function of  $T$  and  $r - n$ 

$r - n$	$V_{\text{out}} @$ $T = -55^\circ\text{C}$	$V_{\text{out}} @$ $T = 50^\circ\text{C}$	$V_{\text{out}} @$ $T = 150^\circ\text{C}$	Maximum error
1	1.226	1.228	1.227	2 mV
2	1.252	1.256	1.253	4 mV
3	1.279	1.284	1.280	5 mV
4	1.305	1.312	1.307	7 mV
5	1.331	1.339	1.333	8 mV

to just tens of millivolts out of a total that is greater than a volt. Hence, the output need only be trimmed to a value a few percent greater than  $V_{G0}$  at the temperature where zero TC is desired (generally, the center of the operating temperature range).

At this point, we'd like to quantify the errors that are caused by the curvature. Unfortunately, although the equations we've developed so far are valuable for design, they aren't quite suitable for analysis. To derive one that is, let us choose the factor  $m$  so that the output voltage has zero TC at some temperature we'll call  $T_R$  (for the reference temperature). Throughout, we'll use the subscript  $R$  to denote a variable's value at this reference temperature. With this notational convention, we may express  $V_{\text{out}}$  as follows:

$$V_{\text{out}}(T) = V_{G0} + \frac{T}{T_R}(r - n)V_{TR} - \frac{T}{T_R}(r - n)V_{TR} \ln\left(\frac{T}{T_R}\right), \quad (14)$$

or, as some prefer,

$$V_{\text{out}}(T) = V_{G0} + \frac{T}{T_R}(r - n)V_{TR} \left[1 - \ln\left(\frac{T}{T_R}\right)\right]. \quad (15)$$

Note that this equation has the right limiting behavior: when  $T = T_R$ , it yields the output voltage corresponding to the zero-TC condition. Also note that, if we were able to arrange for the collector currents to vary as  $T^n$  with  $n = r$ , then the output voltage would have zero TC at all temperatures if  $V_{\text{out}}$  were adjusted to a value  $V_{G0}$  at any temperature. This last observation is at the core of many efforts to synthesize curvature-corrected bandgap references.

Even without elaborate curvature-correction methods, though, the Brokaw cell (where  $n = 1$  in the classic implementation) provides outstanding performance; the curvature inherent in bipolars is simply not all that bad, and the Brokaw cell contributes little error of its own. To illustrate this point, let's compute the actual error one could expect, over a temperature range of  $-55^\circ\text{C}$  to  $+150^\circ\text{C}$ , if  $T_R$  is chosen as  $+50^\circ\text{C}$  and if the quantity  $r - n$  ranges from 1 to 5; see Table 10.1.

As is evident, the total change in output voltage is less than a percent over the entire temperature range, even with relatively large values of  $r - n$ . Furthermore, the output is a maximum at the reference temperature, and drops off above and below this temperature in a quasiparabolic manner. As a consequence, setting  $T_R$  equal to



 


FIGURE 10.9. CMOS bandgap reference.

the center of the desired operating temperature range nearly minimizes the maximum deviation from the value at  $T_R$ .

As a final note, the levels of performance in Table 10.1 assume an ideal scenario in which second-order errors (due to device mismatch, nonzero resistor TC,  $\beta$  drift, etc.) are ignored. Actual performance will be somewhat worse in practice owing to the combined effect of these sources. Careful layout of all devices is mandatory in order to minimize errors.

### 10.5.2 BANDGAP REFERENCES IN CMOS TECHNOLOGY

The classic Brokaw cell uses bipolar transistors in which all device terminals float, so it cannot be implemented directly in this form in CMOS technology. Rearranging to accommodate the restrictions placed on the parasitic substrate p–n–p yields the circuit shown in Figure 10.9.

Transistor  $Q_2$  is designed to have  $m$  times the emitter area of  $Q_1$ . The quad of CMOS transistors enforces equal emitter currents, so that the collector current density ratio is approximately  $m$ . Implicit in the last statement is that this circuit has a greater sensitivity to  $\beta$  than the original Brokaw cell. This unfortunate consequence of being forced to use the substrate p–n–p's leads to larger errors than the classic bandgap cell, particularly because  $\beta$  is rarely large enough to be ignored (values of 5–10 are typical). Nevertheless, even a poorly performing bandgap reference is considerably superior to anything that can be built out of pure CMOS components.

Choosing component values for this circuit proceeds in a manner quite similar to that for the classic cell. Begin by specifying a reference temperature  $T_R$  at which the TC is to be zero. For illustrative purposes, assume that this temperature is to be 350 K.

The next step is to calculate the target output voltage at this reference temperature. As mentioned previously, the shallow, heavily doped p+ diffusions used to make the emitters lead to relatively large curvature coefficients, with  $r$  typically 4 or 5. If no

device models a  
the quantity  $r$  –

Now assume  
and that the larg  
is simply

If we assume a

thus completin

As a final co  
tively constant  
offsets the PT/  
to the PMOS n  
justed through  
a bias current r

As a final co  
the relatively p  
errors. Using l  
beneficial, but  
as switches, al  
supposed to m  
every alternati  
example, then  
technique, unt  
CMOS proces  
plementations

A constant cu  
case. Importa  
must be held c

A circuit w  
a reference re  
we've already

<sup>10</sup> V. Ceekala et  
Digest of Tec  
2001, grantec

device models are available, a reasonable starting point is to assume a value of 4 for the quantity  $r - n$ . Hence, the target output voltage should be

$$V_{\text{out}} = V_{G0} + (r - n)V_T \approx 1.32 \text{ V.} \quad (16)$$

Now assume that we have selected 100  $\mu\text{A}$  for the individual emitter currents and that the larger transistor,  $Q_2$ , has a  $V_{\text{BE}}$  of 0.65 V at this current at  $T_R$ . Then  $R_2$  is simply

$$R_2 = \frac{V_{\text{out}} - V_{\text{BE}2}}{I_E} = 6.7 \text{ k}\Omega. \quad (17)$$

If we assume an  $m$  equal to 8 then  $V_{\text{BE}1}$  is about 63 mV larger than  $V_{\text{BE}2}$ . Hence,

$$R_1 = \frac{V_{\text{out}} - V_{\text{BE}1}}{I_E} = 6.07 \text{ k}\Omega, \quad (18)$$

thus completing the design.

As a final comment on this circuit, one usually finds that the bias current is relatively constant with temperature because resistors typically have a positive TC, which offsets the PTAT tendency of the core design. Thus, currents from a mirror slaved to the PMOS mirror will be roughly constant. The precise TC obtained may be adjusted through a suitable choice of resistor values if the ultimate goal is to generate a bias current rather than a reference voltage.


As a final comment on CMOS bandgap circuits in general, it must be noted that the relatively poor matching that CMOS normally exhibits can result in significant errors. Using large devices and operating them at moderately high gate overdrives is beneficial, but it costs power. An alternative technique is to make use of MOSFETs as switches, alternately exchanging the left and right transistors of every pair that is supposed to match.<sup>10</sup> By symmetry, the effect of mismatch should reverse sign at every alternation. If we simply time-average the output with a low-pass RC filter, for example, then the output voltage will be insensitive to offset, to first order. Using this technique, untrimmed  $3\sigma$  errors of about 1% have been demonstrated in a 0.18- $\mu\text{m}$  CMOS process. Such performance is competitive with many trimmed bipolar implementations. This general technique may be applied wherever symmetry allows it.

## 10.6 CONSTANT- $g_m$ BIAS

A constant current or constant voltage is often desirable, but this is not always the case. Important examples include situations in which it is the transconductance that must be held constant, such as in the low-noise amplifiers described in Chapter 12.

A circuit whose bias current corresponds to a  $g_m$  that is inversely proportional to a reference resistance is a modification of the self-biased CMOS quad of transistors we've already seen; this is shown in Figure 10.10.

<sup>10</sup> V. Ceekala et al., "A Method for Reducing the Effects of Random Mismatch in CMOS," *ISSCC Digest of Technical Papers*, February 2002. Also see U.S. Patent #6,535,054, filed 20 December 2001, granted 18 March 2003.

 FIGURE 10.10. Basic constant- $g_m$  reference.

To derive an expression for the transconductance of  $M_1$ , first use KVL to write

$$V_{gs1} = V_{gs2} + IR_2 \implies V_{od1} = V_{od2} + IR_2, \quad (19)$$

where we have assumed perfect PMOS mirrors and equal threshold voltages for the two long-channel NMOS transistors.

If transistor  $M_2$ 's width is  $m$  times that of  $M_1$ , then the two overdrive voltages are related as follows:

$$V_{od2} = \frac{V_{od1}}{\sqrt{m}}. \quad (20)$$

For the long-channel devices we have been considering all along,  $g_m$  is simply  $2I/V_{od}$ . Therefore,

$$V_{od1} = V_{od2} + IR_2 \implies V_{od1} = \frac{V_{od1}}{\sqrt{m}} + IR_2 \implies \frac{2I}{g_{m1}} = \frac{2I}{\sqrt{m}g_{m1}} + IR_2. \quad (21)$$

Solving for the transconductance yields

$$g_{m1} = \frac{2(1 - 1/\sqrt{m})}{R_2}, \quad (22)$$

revealing explicitly that the transconductance is proportional to the reciprocal of reference resistance  $R_2$ . If the ratio  $m$  is precisely 4, then the proportionality becomes an equality. The currents  $I_{REFN}$  and  $I_{REFP}$  generated by this cell may be mirrored to slave devices (with or without scaling) to set the transconductance of multiple NMOS devices in other parts of a circuit.



Because this bias generator depends on the quality of the reference, demanding applications may require the use of an external resistance. In noncritical applications, ordinary on-chip resistances (e.g., unsilicided poly) may suffice.

The foregoing development rather optimistically assumes that both NMOS transistors possess the same threshold voltages, despite the unequal source-to-bulk potentials for the devices. In practice, the back-gate bias effect produces unequal threshold shifts and thus introduces an error. To minimize the impact of this back-gate effect, choose relatively high current densities for the devices – within the constraints of maintaining long-channel operation. Doing so assures large overdrives, making the overall

circuit's behavior low  $IR_2$  products. These strategies are largely irrelevant for resistor  $R_2$  equal to  $M_3$ . The current is a level shift equal to

$$V_{gs1} -$$

Because of this circuit's low  $IR_2$  products, mismatch errors are small. Matching the overdrives. Since the overdrives are close to equal

  FIGURE 10.11. Improved constant- $g_m$  reference.FIGURE 10.12. Minimum-error constant- $g_m$  reference.

circuit's behavior less sensitive to threshold differences. Finally, select a relatively low  $IR_2$  product to minimize the difference in source-to-bulk voltages. Use of both of these strategies together usually permits the attainment of satisfactory performance.

An alternative constant- $g_m$  reference is shown in Figure 10.11. In this circuit,  $M_2$  is largely irrelevant, thanks to the op-amp. As seen in the figure, the voltage across resistor  $R_2$  equals  $M_1$ 's  $V_{gs}$  level-shifted downward by an amount equal to the  $V_{gs}$  of  $M_3$ . The current  $I_{bias3}$  is chosen in conjunction with the dimensions of  $M_3$  to produce a level shift equal to the threshold voltage of  $M_1$ . Therefore,

$$V_{gs1} - V_{gs3} \approx V_{gs1} - V_{t1} \approx IR_2 \Rightarrow \frac{2I}{g_{m1}} \approx IR_2 \Rightarrow g_{m1} \approx \frac{2}{R_2}. \quad (23)$$

Because of the additional degree of freedom represented by  $I_{bias3}$ , it is possible for this circuit to exhibit smaller errors than the previous one without requiring small  $IR_2$  products. Still, operation of  $M_1$  with large overdrives remains beneficial.

Mismatched mirrors are an additional error source in a great many analog circuits. Matching may be improved by using large devices biased at reasonably large overdrives. Systematic mismatch is reduced if the drain-source voltages are made as close to equal as possible. The circuit in Figure 10.12 uses another op-amp to force

operation of the PMOS mirror transistors with nominally equal drain-source voltages, thereby eliminating systematic errors due to channel-length modulation and DIBL.

With a constant- $g_m$  circuit, one may reduce greatly the variation in  $g_m$ -dependent parameters – such as gain, input impedance, and noise figure of LNAs – as temperature, processing, and supply voltage vary.

## 10.7 SUMMARY

We have seen that the self-biased cell is quite versatile, permitting the generation of currents proportional to the ratio of a voltage in one branch to the resistance in the other. The voltage may be provided by a variety of elements, such as a forward-biased junction. Although a  $V_{BE}$  by itself has limited utility as a voltage reference because of its negative TC, its CTAT behavior is valuable in compensating the PTAT  $\Delta V_{BE}$  in a bandgap reference circuit to yield an output roughly equal to  $V_{G0}$  with extremely small temperature variation. Even when parasitic bipolars are used in an otherwise CMOS circuit, the bandgap principle allows the synthesis of more accurate and stable voltages or currents than is possible with ordinary CMOS circuits.

Finally, a constant- $g_m$  bias circuit was presented, allowing the stable biasing of such transconductance-sensitive circuits as filters and LNAs.

## PROBLEM SET FOR VOLTAGE REFERENCES AND BIASING

**PROBLEM 1** This problem explores in more detail the characteristics of the constant- $g_m$  reference. Refer to Figure 10.13.

Rather than choosing  $m = 4$ , consider simply making  $m$  very large. In the limit, the transconductance approaches a value that is twice what is obtained when  $m = 4$ . Show this formally by deriving an expression for the transconductance of  $M_1$  if the  $M_2$  is  $S$  times as wide as  $M_1$ . To simplify the derivation, neglect body effect and assume that the PMOS mirror is an ideal 1 : 1 mirror.

 


FIGURE 10.13. Basic constant- $g_m$  reference.

**PROBLEM 2** In effect of PMOS PMOS devices : length modulating ductance of  $M_1$ ,

**PROBLEM 3** I resistor value to 1 mS at 300 K. SPICE to verify

**PROBLEM 4** take finite p–n–tors are often be

**PROBLEM 5** age reference i shown in Figur 3 V. Use the lev

**This Page is Inserted by IFW Indexing and Scanning  
Operations and is not part of the Official Record**

**BEST AVAILABLE IMAGES**

Defective images within this document are accurate representations of the original documents submitted by the applicant.

Defects in the images include but are not limited to the items checked:

☒ BLACK BORDERS

☒ IMAGE CUT OFF AT TOP, BOTTOM OR SIDES

☐ FADED TEXT OR DRAWING

☐ BLURRED OR ILLEGIBLE TEXT OR DRAWING

☐ SKEWED/SLANTED IMAGES

☐ COLOR OR BLACK AND WHITE PHOTOGRAPHS

☐ GRAY SCALE DOCUMENTS

☐ LINES OR MARKS ON ORIGINAL DOCUMENT

☐ REFERENCE(S) OR EXHIBIT(S) SUBMITTED ARE POOR QUALITY

☐ OTHER: \_\_\_\_\_

**IMAGES ARE BEST AVAILABLE COPY.**

**As rescanning these documents will not correct the image problems checked, please do not report these problems to the IFW Image Problem Mailbox.**